


Lecture 23, Mar 11, 2022

Series and Parallel Connections of Capacitors

- Suppose we have n capacitors c_1, \dots, c_n connected in parallel
 - Each capacitor has a current $i_k = c_k \frac{dv_k}{dt}$ but the capacitors all have the same voltage, so $i_k = c_k \frac{dv}{dt}$
 - To find the equivalent capacitance, we need to find the total current
 - $i_{tot} = \sum_{k=1}^n i_k = \frac{dv}{dt} \sum_{k=1}^n c_k \implies c_{eq} = \sum_{k=1}^n c_k$
- The equivalent capacitance for capacitors in parallel is the sum of all the capacitances
- Suppose we have n capacitors c_1, \dots, c_n connected in series
 - All capacitors have the same current and each has a voltage v_k
 - KVL gives $v_{tot} = \sum_{k=1}^n v_k \implies \frac{dv_{tot}}{dt} = \sum_{k=1}^n \frac{dv_k}{dt} = \sum_{k=1}^n \frac{1}{c_k} i = i \sum_{k=1}^n \frac{1}{c_k} \implies \frac{1}{c_{eq}} = \sum_{k=1}^n \frac{1}{c_k}$
- The equivalent capacitance for capacitors in series is the reciprocal of the sum of the reciprocals of the capacitances
 - For c_1 and c_2 in series, $c_{eq} = \frac{c_1 c_2}{c_1 + c_2}$
- The behaviour in series vs parallel for capacitors is opposite that of resistors

Inductors

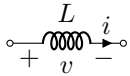- An inductor consists of a coil of conducting wire with a core of any material
- Like a capacitor, an inductor stores energy, this time in a magnetic field generated as current passes through it
 - Since the energy density for a magnetic field is much larger than that of an electric field, the energy that can be stored in an inductor is much larger than a capacitor
- Inductor symbol:



- For an inductor, voltage is related to current by $v = L \frac{di}{dt}$; an inductor is the dual of a capacitor
 - L is the *inductance* and has units of henry H
 - * The larger the value of L , the more energy can be stored in the inductor
 - * L depends on the kind of core used in the inductor
 - This relation only holds if PSC holds
- To get current from voltage we can integrate: $i(t_2) = i(t_1) + \frac{1}{L} \int_{t_1}^{t_2} v dt$ or $i(t) = i(0) + \frac{1}{L} \int_0^t v(\tau) d\tau$
- Properties of inductors:
 1. If the current is constant, then the voltage is always 0
 - In a DC circuit (in steady state) the inductor can be modelled by a short
 2. The current of an inductor cannot change abruptly since that would create an infinite voltage

- Energy of a capacitor: $W(t_2) - W(t_1) = \int_{t_1}^{t_2} P(t) dt$
$$= \int_{t_1}^{t_2} v(t)i(t) dt$$
$$= \int_{t_1}^{t_2} Li(t) \frac{di}{dt} dt$$
$$= L \int_{t_1}^{t_2} i di$$
$$= \frac{1}{2}L(i^2(t_2) - i^2(t_1))$$

- Assuming no magnetic field at $t = 0$, $W(t) = \frac{1}{2}Li^2(t)$
 - Like an ideal capacitor, an ideal inductor does not dissipate energy and only stores it
- The equivalent inductance of inductors in series is the sum of the inductances; in parallel it's the reciprocal of the sum of the reciprocals (like resistors)